

Lab Exercise 7

7.1 Structural Description of 1 Bit Full Adder


7.1.1 Truth Table

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

7.1.2 Verilog Code:

```
module fulladd (cin, x,y,s,cout);  
input cin,x,y;  
output s, cout;  
wire z1,z2,z3;  
xor (s,x,y,cin);  
and (z1,x,y);  
and(z2, x,cin);  
and (z3,y,cin);  
or (cout, z1,z2,z3);  
endmodule
```

7.1.3 Vector Waveform

 


7.2 Behavioral Description of 1-bit Full Adder

7.2.1 Verilog Code:

```
module fulladd_behav(cin,xx,yy,s,cout,LED_COM);
    input cin,xx,yy;
    output cout,s;
    inout LED_COM;
    assign s=xx^yy^cin;
    assign cout=(xx&yy)|(xx&cin)|(yy&cin);
    assign LED_COM=1;
endmodule
```

7.2.2 Vector Waveform

 

7.3 Behavioral Description of 4 Bit Full Adder

7.3.1 Truth Table


[illegible]

7.3.2 Verilog Code

```
module adder4(carryin, x3,x2,x1,x0,y3,y2,y1,y0,s3,s2,s1,s0,carryout,LED_COM);
    input carryin, x3,x2,x1,x0,y3,y2,y1,y0;
    output s3,s2,s1,s0,carryout;
    inout LED_COM;
    wire c1,c2,c3;
    fulladd stage0 (carryin, x0,y0,s0,c1);
    fulladd stage1 (c1, x1,y1,s1,c2);
    fulladd stage2 (c2, x2,y2,s2,c3);
    fulladd stage3 (c3, x3,y3,s3,carryout);
    assign LED_COM=1;
endmodule

module fulladd(cin,xx,yy,s,cout);
    input cin,xx,yy;
    output cout,s;
    assign s=xx^yy^cin;
    assign cout=(xx&yy)|(xx&cin)|(yy&cin);
endmodule
```

7.3.3 Vector Waveform

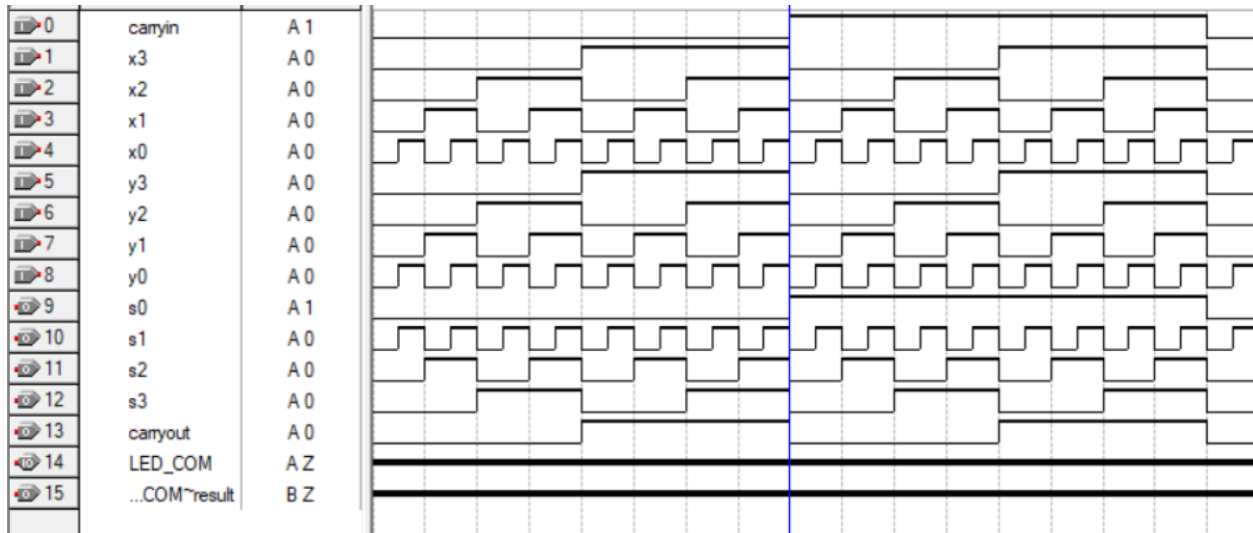

Lab Exercise 8

8.1 Verilog Code

```
module addsub(cin, x3,x2,x1,x0,y3,y2,y1,y0,s3,s2,s1,s0,cout, LED_COM);
input cin, x3,x2,x1,x0,y3,y2,y1,y0;
output s3,s2,s1,s0,cout;
inout LED_COM;
wire c1,c2,c3,yy0, yy1, yy2,yy3;
adsub(cin, y3,y2,y1,y0,yy0, yy1, yy2,yy3);
fulladd stage0 (cin, x0,y0,s0,c1);
fulladd stage1 (c1, x1,y1,s1,c2);
fulladd stage2 (c2, x2,y2,s2,c3);
fulladd stage3 (c3, x3,y3,s3,cout);
assign LED_COM=1;
endmodule
```

```
module fulladd(cin,xx,yy,s,cout);
input cin,xx,yy;
output cout,s;
assign s=xx^yy^cin;
assign cout=(xx&yy)|(xx&cin)|(yy&cin);
endmodule
```


```
module adsub(cin, y3,y2,y1,y0,yy0, yy1, yy2,yy3);
input cin, y0, y1, y2, y3;
output yy0, yy1, yy2, yy3;
assign yy0 = cin^y0;
assign yy1 = cin^y1;
```

```


assign yy2 = cin^y2;
assign yy3 = cin^y3;
endmodule

```

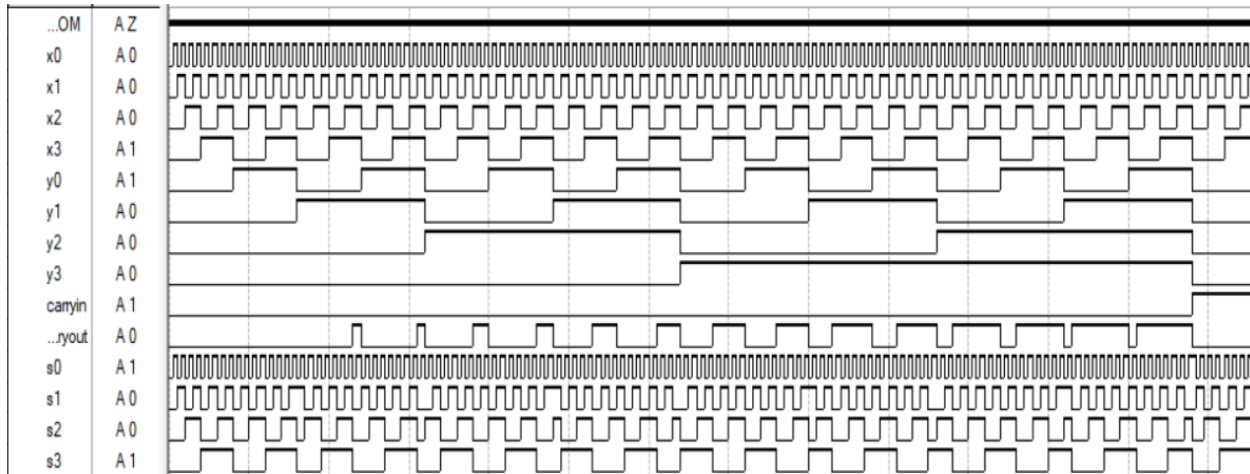8.2 Vector Waveform for Addition (Cin = 0)



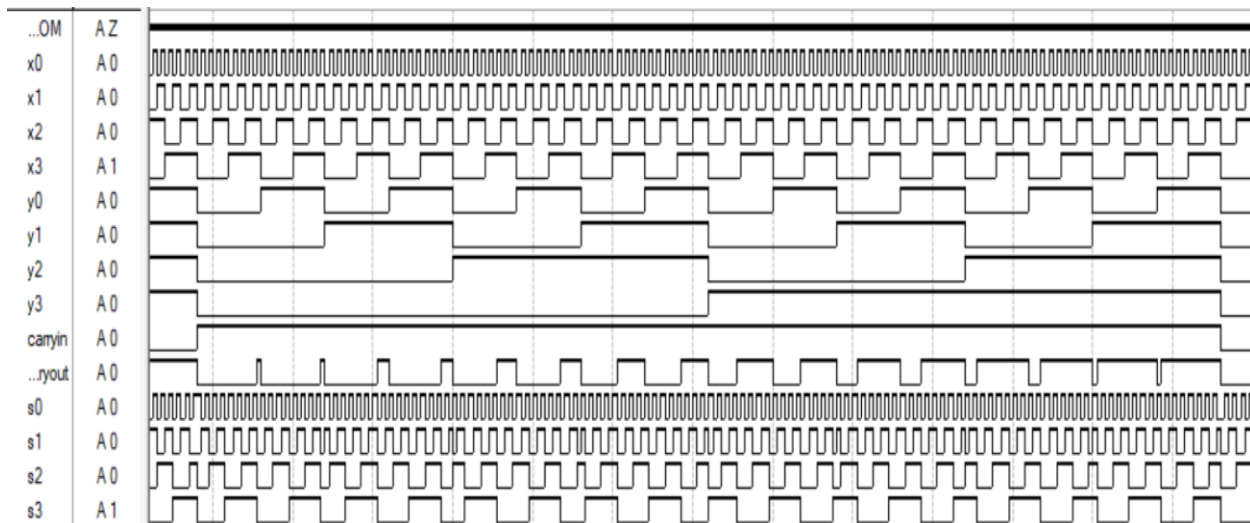
8.3 Vector Waveform Subtraction (Cin = 1)




Report Problem 1

12 Bit Comparator


R.1.1 $A > B$

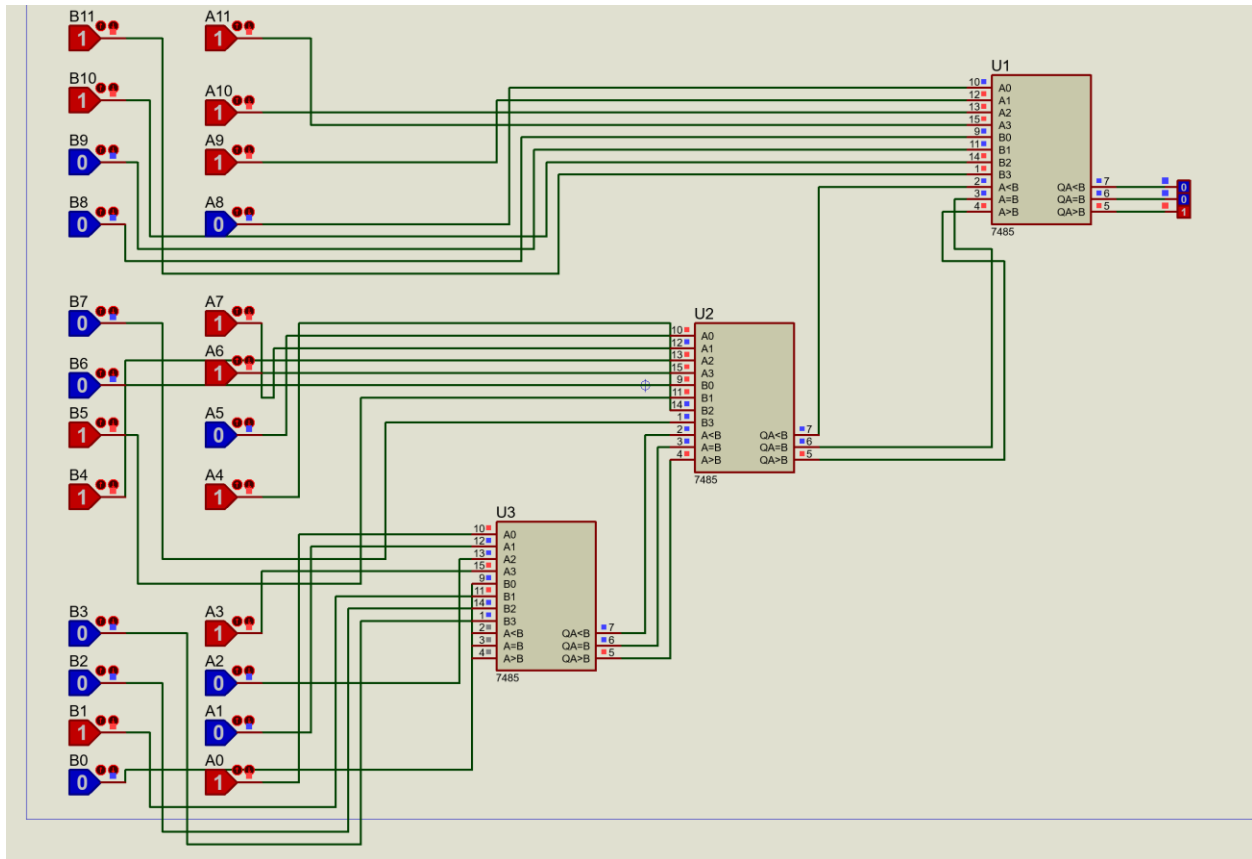

R.1.2 $A < B$

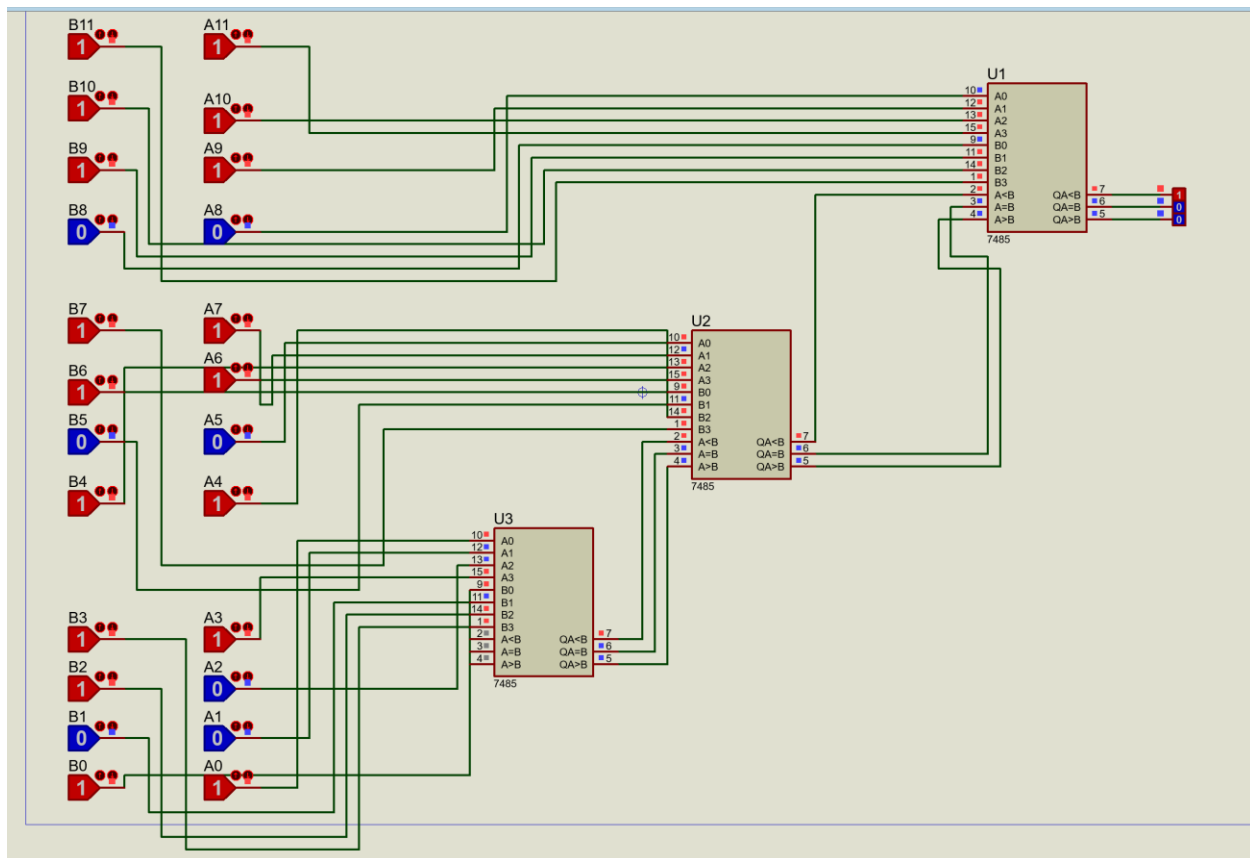

R.1.3 A = B

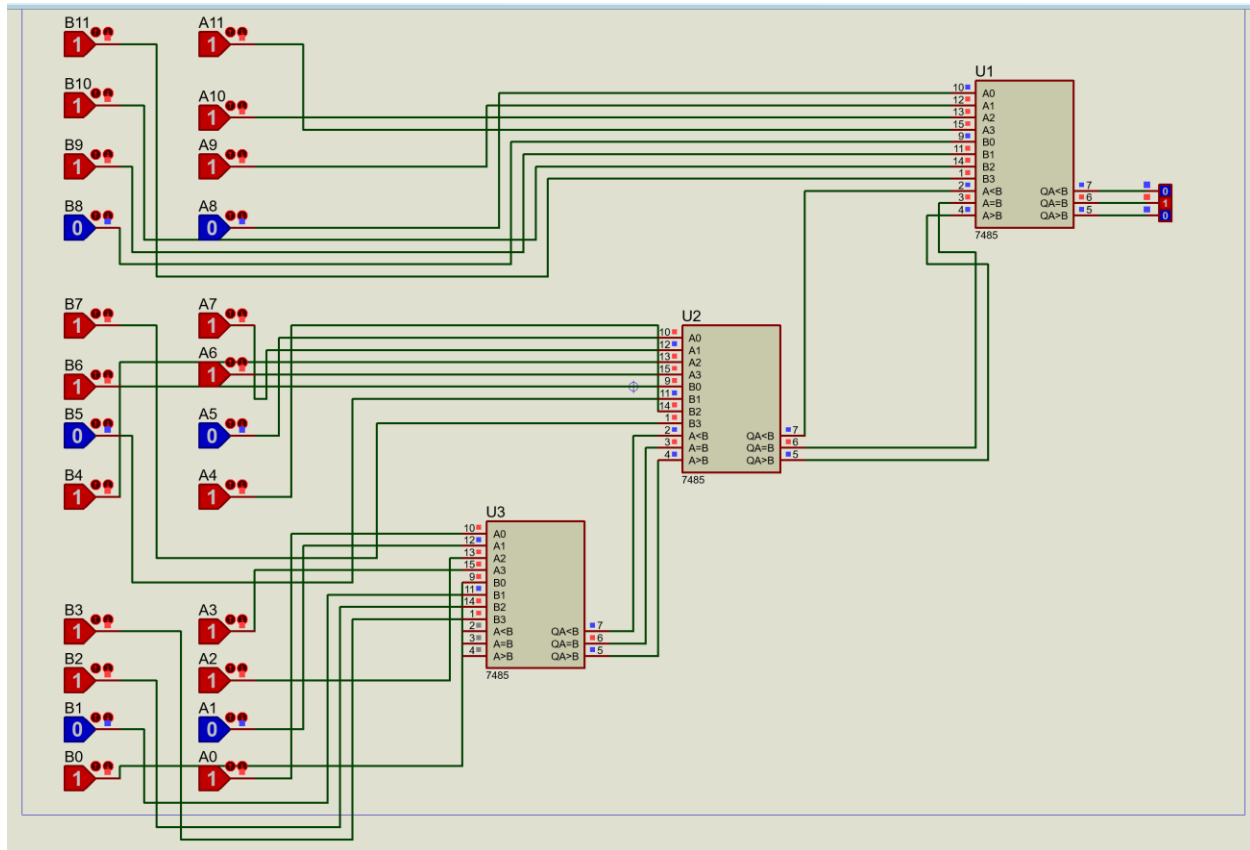

Report Problem 2

Ternary Adder


R.2.1 Binary Encoded Truth Table

A1	A0	B1	B0	S1	S0	C
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
1	0	0	0	1	0	0
1	0	0	1	0	0	1
1	0	1	0	0	1	1

R.2.2 Verilog Code

```
module ternaryadd(c, a0, a1, b0, b1, s0, s1, LED_COM);  
input a0, a1, b0, b1;  
wire x0, y0, x1, y1;  
output s0, s1, c;  
inout LED_COM;  
assign x0 = !a0;  
assign x1 = !a1;  
assign y0 = !b0;  
assign y1 = !b1;  
assign s0 = (x1 & x0 & b0) | (a0 & y1 & y0) | (a1 & b1);  
assign s1 = (x1 & x0 & b1) | (a1 & y1 & y0) | (a0 & b0);  
assign c = (a0 & b1) | (a1 & b1) | (a1 & b0);  
assign LED_COM = 1;  
endmodule
```

R.2.3 Vector Waveform

 

R.2.4 K-Map and Boolean Expression for S0:

Karnaugh Map

<i>f</i>		<i>B1,B0</i>			
		00	01	11	10
<i>A1,A0</i>	00	0	1	-	0
	01	1	0	-	0
	11	-	-	-	-
	10	0	0	-	1

$$f(A1, A0, B1, B0) = A1'A0'B0 + A0B1'B0' + A1B1$$

R.2.5 K-map and Boolean Expression for S1:

Karnaugh Map

f		$B1, B0$			
		00	01	11	10
$A1, A0$	00	0	0	-	1
	01	0	1	-	0
	11	-	-	-	-
	10	1	0	-	0

$$f(A1, A0, B1, B0) = A1'A0'B1 + A0B0 + A1B1'B0'$$

R.2.6 K-map and Boolean Expression for C:

Karnaugh Map

f		$B1, B0$			
		00	01	11	10
$A1, A0$	00	0	0	-	0
	01	0	0	-	1
	11	-	-	-	-
	10	0	1	-	1

$$f(A1, A0, B1, B0) = A0B1 + A1B0 + A1B1$$